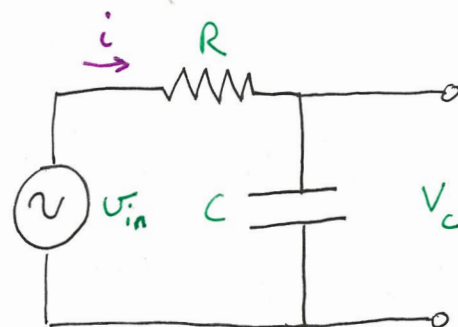


Lecture 19 - RC, RL, RLC ac circuits

The RC circuit (exponential analysis)

We want to find the voltage amplitude V_c across the capacitor.

Procedure:



- Apply voltage $v_{in} = V_0 \cos(\omega t)$
- Use complex notation $v_{in} = V_0 \operatorname{Re}(e^{j\omega t})$ temporarily dropping the "Re".
- Write down the voltage loop rule using $v_x = i z_x$ for each circuit element.
- Add impedance in circuits just like resistance.
- Solve for i ; solve for v_c as a function of ω .

In circuit above with $v_{in} = V_0 e^{j\omega t}$:

- Loop rule: $v_{in} - v_c - v_R = v_{in} - i z_c - i z_R = 0$

$$v_{in} = i \left(\frac{1}{j\omega C} + R \right)$$

- $$i(t) = \frac{v_{in}}{R + \frac{1}{j\omega C}} = \frac{v_{in} (R - \frac{1}{j\omega C})}{(R + \frac{1}{j\omega C})(R - \frac{1}{j\omega C})} = v_{in} \frac{R + \frac{j}{\omega C}}{(\frac{1}{\omega C})^2 + R^2}$$

Note: Resistor in-phase with driving voltage. $i(t)$ is $-\frac{\pi}{2}$ out of phase.

$$\bullet I = (i \cdot i^*)^{1/2} = v_{in} \frac{1}{[R^2 + (\frac{1}{\omega C})^2]^{1/2}}$$

$$\bullet v_c = iX_c = v_{in} \frac{(R + \frac{j}{\omega C})(-\frac{1}{\omega C})}{R^2 + (\frac{1}{\omega C})^2}$$

Interpretation:

There are two parts to the current response, i.e., in- and out of phase with the applied voltage.

The signal current:

$$i = v_{in} \frac{R + j/\omega C}{R^2 + (\frac{1}{\omega C})^2} = \frac{v_{in}}{R} \frac{(R\omega C)^2 + j\omega C}{1 + (R\omega C)^2}$$




is nearly constant at high frequency and is resistor-like because the impedance of the capacitor becomes very small.

At low frequency, the current is controlled by the high impedance of the capacitor.



The overall capacitor voltage magnitude is

$$V_c \text{ GAIN} = g = \left| \frac{V_c}{V_{in}} \right| = \left| \frac{iX_c}{V_{in}} \right| = \left| \frac{1}{(1 + j\omega RC)} \right| = \sqrt{\frac{1}{1 + (\omega RC)^2}}$$

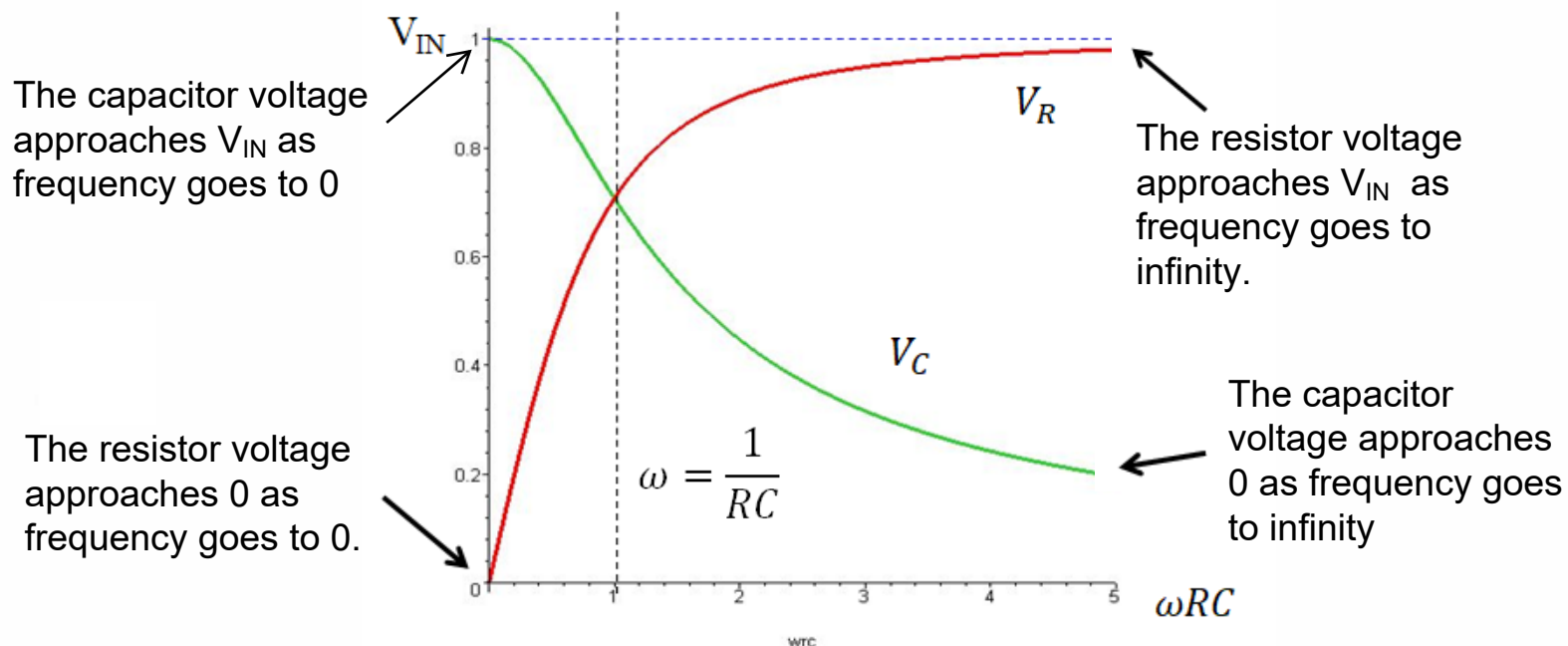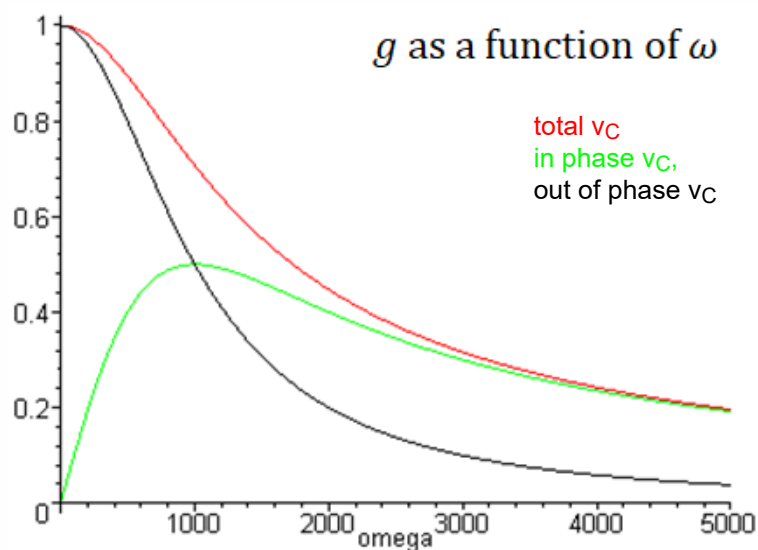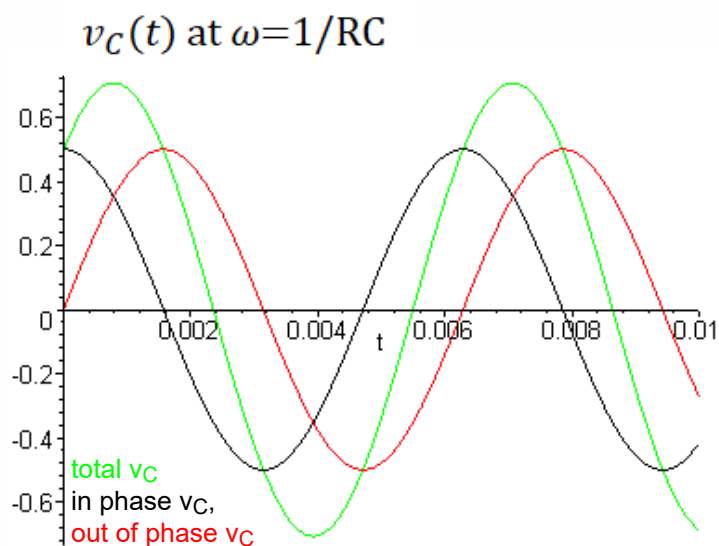Voltage across the capacitor in an RC circuit



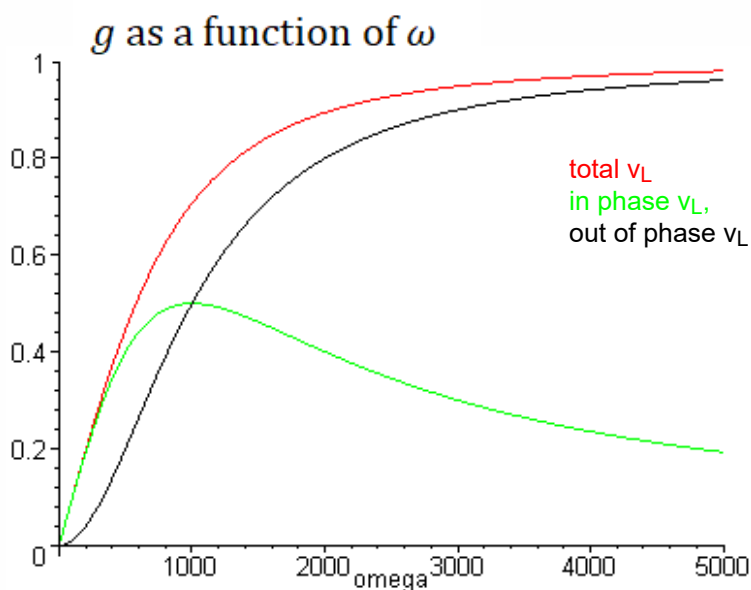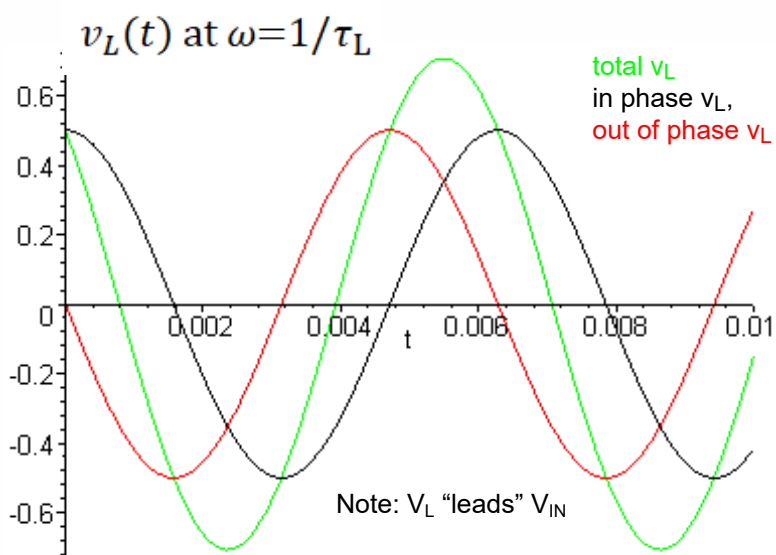Voltage across the capacitor in an RL circuit




The RL circuit (exponential analysis)

We want to find the voltage amplitude V_L across the inductor.

Procedure :

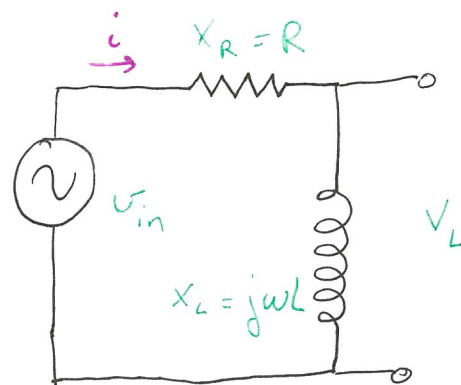- Apply voltage $v_{in} = V_0 \cos(\omega t)$
- Write down voltage loop rule using $v_k = i z_k$ for each circuit element.
- Solve for i , then I .
- Solve for V_L as a function of ω .



Here : $v_{in} = i z = i R + j\omega L$

$$\Rightarrow i(t) = \frac{v_{in}}{R + j\omega L} = \frac{v_{in}/R}{1 + j\omega L/R}$$

$$v_L(t) = i z_L = i j\omega L = \frac{v_{in} j\omega L/R}{1 + j\omega L/R} = \frac{v_{in} (j\omega \tau_L + \omega^2 \tau_L^2)}{(1 + \omega^2 \tau_L^2)}$$


$$g_L = \frac{V_L}{V_{in}} \frac{\omega \tau_L}{\sqrt{1 + (\omega \tau_L)^2}} \quad \text{with} \quad \tau_L = \frac{L}{R}$$

The RLC circuit (exponential analysis)

5

Loop equation using impedance:
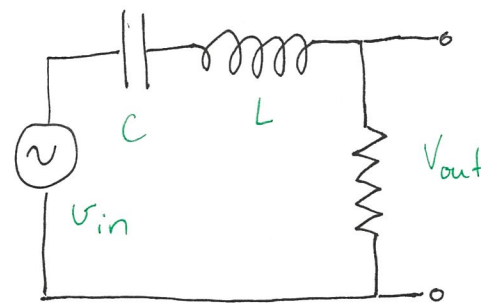
$$V_{in} e^{j\omega t} = \frac{1}{j\omega C} i + j\omega L i + R i$$



$$\Rightarrow i(t) = \frac{V_{in} e^{j\omega t}}{-\frac{j}{\omega C} + j\omega L + R}$$

$$V_{out} = R i = V_{in} e^{j\omega t} \frac{R}{j\left(\omega L - \frac{1}{\omega C}\right) + R}$$


$$\frac{V_{out}}{V_{in}} = \frac{1 - j\left(\omega \frac{L}{R} - \frac{1}{\omega RC}\right)}{1 + \left(\omega \frac{L}{R} - \frac{1}{\omega RC}\right)^2} ; \quad g = \sqrt{\frac{R/L}{\frac{R}{L} + \left(\omega - \frac{1}{\omega LC}\right)^2}}$$

1) When $\omega^2 = \frac{1}{LC} \Rightarrow \omega = \sqrt{\frac{1}{LC}}$ then $\frac{V_{out}}{V_{in}} = 1$

2) When $\omega \rightarrow 0$, then $\frac{V_{out}}{V_{in}} \approx -j\omega RC$

3) When $\omega \rightarrow \infty$, then $\frac{V_{out}}{V_{in}} \approx \frac{j}{\omega L/R}$

RLC current behavior

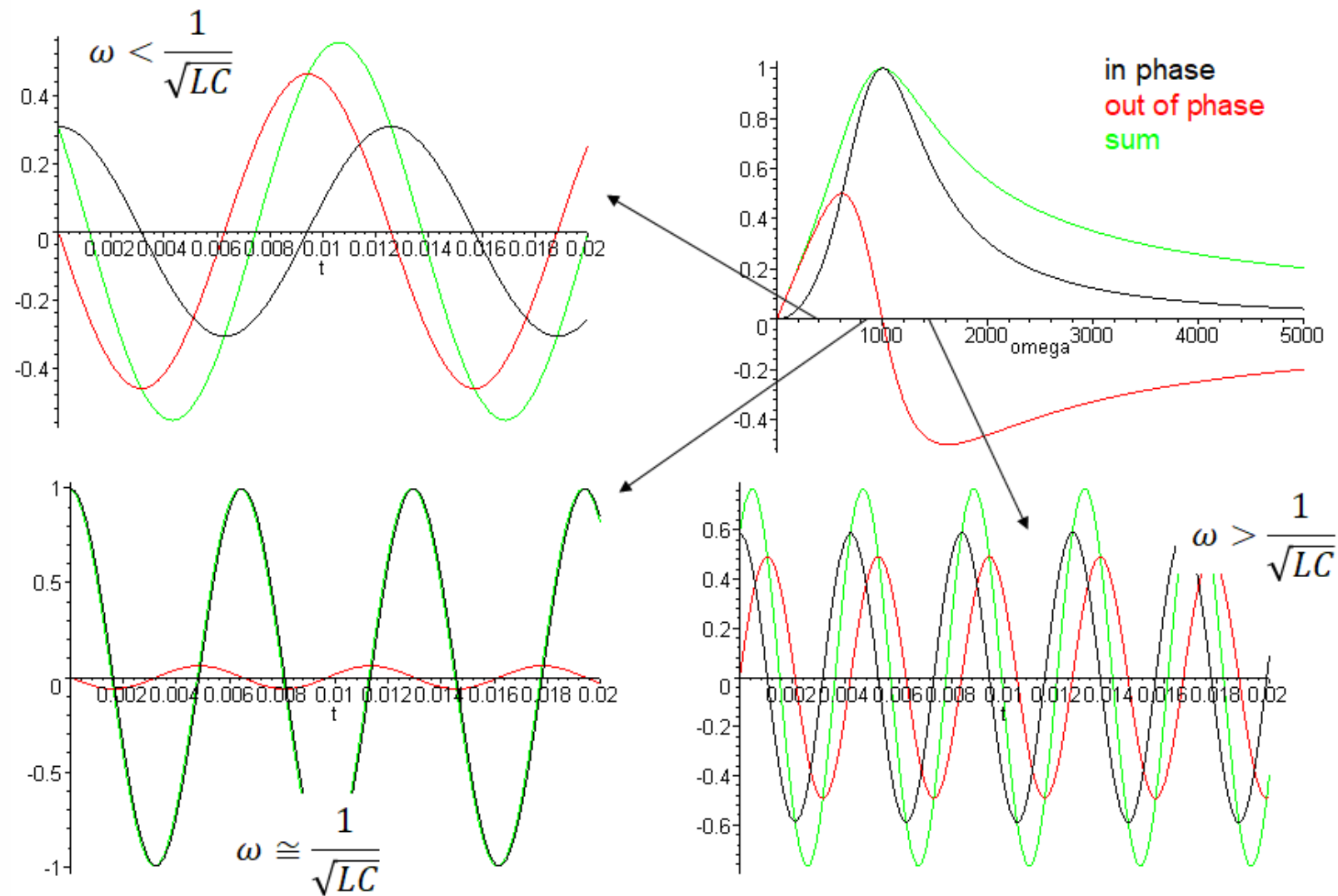

Resonances in the driven RLC circuit

7

At any instant : $v_d(t) = v_R + v_C + v_L = V_d \cos(\omega_d t)$

but v_R , v_C , and v_L have different phases and must be added carefully.

$$I = \frac{V_d}{\sqrt{R^2 + (X_L - X_C)^2}} = \frac{V_d}{\sqrt{R^2 + \left(\omega_d L - \frac{1}{\omega_d C}\right)^2}}$$

When the driving frequency is such that $\left(\omega_d L - \frac{1}{\omega_d C}\right) = 0$, then

$$I = \frac{V_d}{R} \text{ and is a maximum.}$$

The smaller R is, the sharper the maximum.

